

Name: Aditi Saha
ID : 2019-1-60-024
Sub :

Pre-lab Report: 02

Sat ☐ Sun ☐ Mon ☐ Tue ☐ Wed ☐ Thu ☐ Fri ☐
Time : Date : / /

* The circuit produces a high (logic 1) output only when the binary number is greater than 0101_2 . Input: A, B, C, D. Output: F.

1. Prepare a truth table for the given combinational circuit.

A	B	C	D	F(output)
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Truth table for given combinational circuit

Sub : _____

2. Write a simplified sum of products function from the k-map.

The sum of product function is :

$$F_1(A, B, C, D) = \sum (7, 8, 9, 10, 11, 12, 13, 14, 15)$$

CD \ AB	00	01	11	10
00	0	1	3	2
01	4	5	1	1
11	1	1	1	1
10	1	1	1	1

k-map for SOP

→ BC


→ A

So, the simplified SOP function's expression is $= A + BC$; [cost = 2 + 4 = 6]

Now, the AND-OR logic diagram for the simplified SOP function are given below:

Sub :

Time : Date : / /

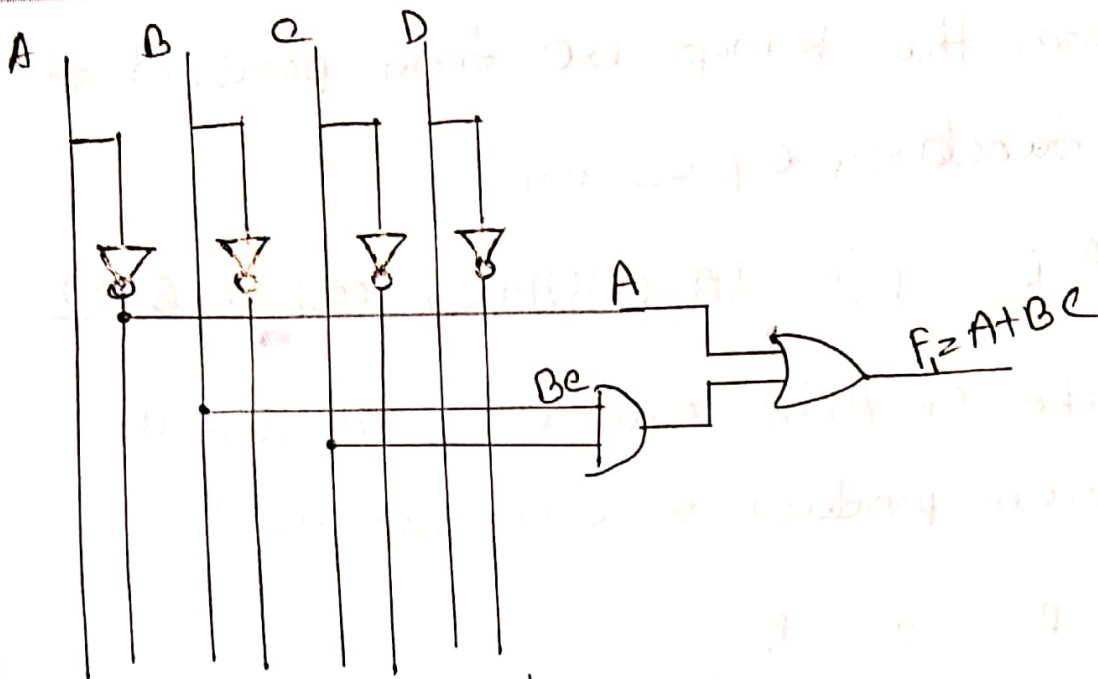

AND-OR logic diagram

3. Write simplified product of sums function from the k-map.

The product of sums (POS) function is :

$F_2(A, B, C, D) = \pi(0, 1, 2, 3, 4, 5)$

	CD	00	01	11	10	
AB	00	0	0	0	0	→ (A+B)
		0	1	3	2	
(A+C)	01	0	0			
		4	5	7	6	
	11					
		12	13	15	14	
	10					
		8	9	11	10	

k-map for POS

Sub :

Sat ☐ Sun ☐ Mon ☐ Tue ☐ Wed ☐ Thu ☐ Fri ☐


Time :

Date : / /

So, from this k-map we find product of sum function's expression:

$$F_2(A, B, C, D) = (A+B)(A+C) \text{ [cost} = 3+6 = 9\text{]}$$

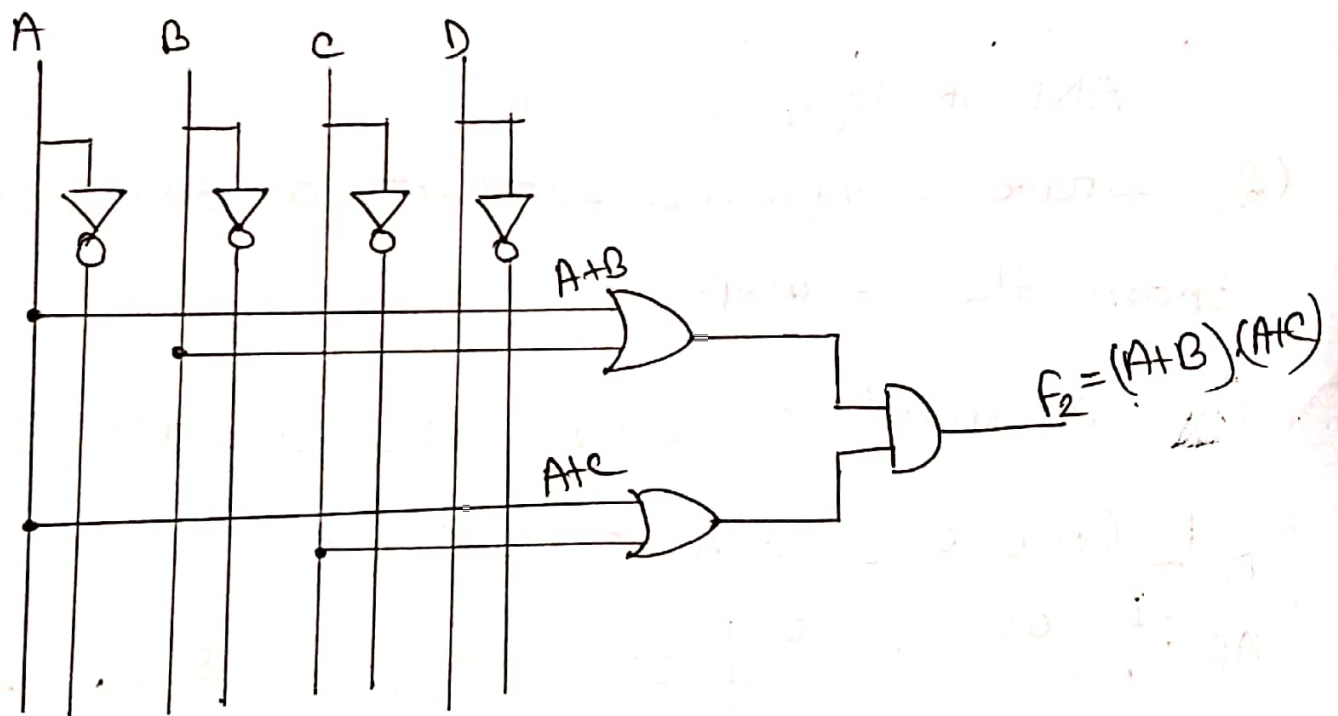Now, the OR-AND logic diagram for the simplified product of sum function:



OR-AND logic diagram