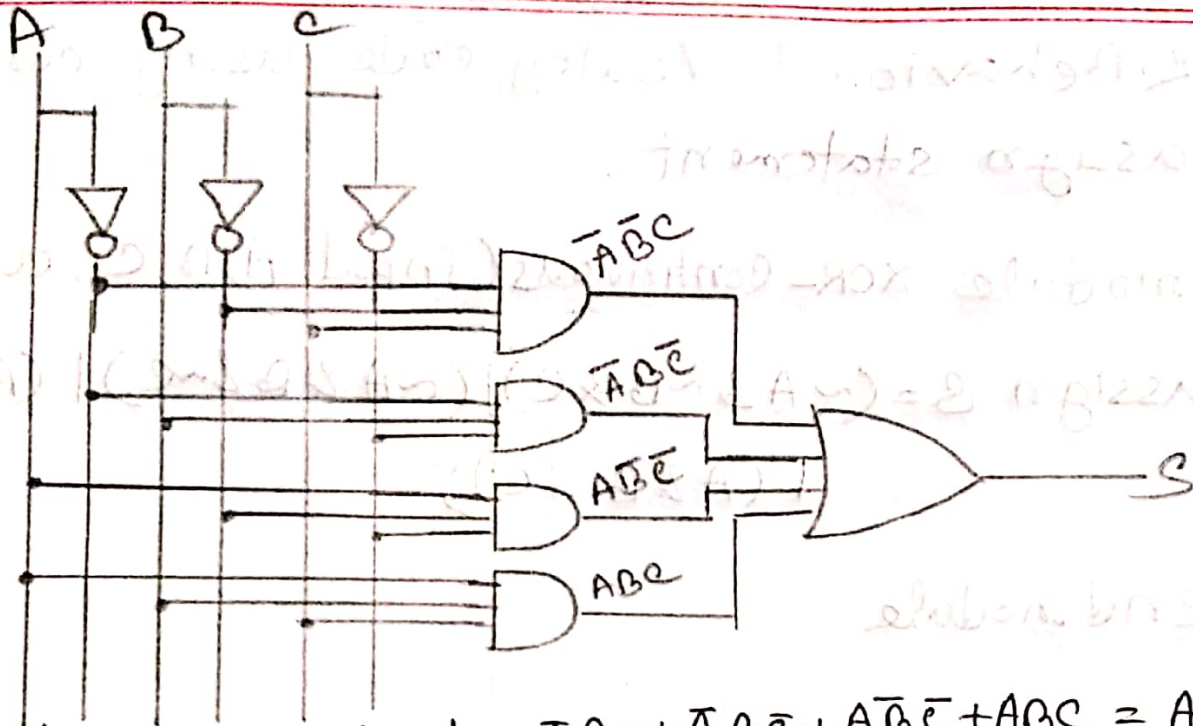


Pre-lab Report-3

Name: Aditi Saha
ID: 2019-1-60-024



Boolean expression is: $AB\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC = A \oplus B \oplus C$
Combinational circuit for 3 input X-OR gate

1. Behavioral code using procedural model.

```
module XOR-Procedural(input A,B,C, output reg S);  
always @(A,B,C)
```

```
begin S=0;
```

```
if (~A & ~B & C) S=1;
```

```
if (~A & B & ~C) S=1;
```

```
if (A & ~B & ~C) S=1;
```

```
if (A & B & C) S=1;
```

```
end
```

```
endmodule
```

2. Behavioral Verilog code using continuous assign statement.

```
module XOR-continuous(input A,B,C, output S);  
assign S = (~A & ~B & C) | (~A & B & ~C) | (A & ~B & ~C)  
           | (A & B & C);  
endmodule
```

Truth Table: Truth table for the given circuit as follows:

A	B	C	S
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1